

Mechatronics for Rehabilitation Engineering: Course Notes

Sivakumar Balasubramanian
CMC Vellore

Update on May 26, 2025

Contents

1	Contents	7
2	Review of Basic Circuit Theory	9
2.1	Basic	9
2.2	Kirchoff's Laws	11
2.3	Series and Parallel Connections	13
2.3.1	Resistors in series and parallel	13
2.3.2	Capacitors in series and parallel	13
2.3.3	Inductors in series and parallel	14
2.3.4	Voltage sources in series and parallel	14
2.3.5	Current sources in series and parallel	14
2.4	Superposition Principle	14
2.5	Practical Voltage and Current Sources	15
2.6	Thevenin's and Norton's Theorems	16
2.7	Maximum Power Transfer Theorem	18
2.8	RC, RL, and RLC Circuits	18
2.9	Steady State Sinusoidal Analysis	21
2.10	Exercise	22
3	Electronics Review	25
3.1	Basic semiconductor concepts	25
3.1.1	Intrinsic semiconductors	25
3.1.2	Doped Semiconductors	26
3.2	Diode	26

List of Figures

2.1	Basic circuit elements: voltage source, current source, resistor, capacitor, and inductor.	9
2.2	A simple electrical circuit with a voltage source, a current source, and a bunch of resistors.	12
2.3	A simple circuit with two sources	15
2.4	Comparison of the voltage-current relationship of an ideal and a practical voltage source.	16
2.5	Thevenin's and Norton's circuits for a complex linear circuit. The Thevenin and Norton equivalent circuits have the same voltage-current relationship for any load.	17
2.6	Maximum power transfer theorem.	18
2.7	Simple RC and RL circuits and their transient responses.	20
2.8	A simple RLC circuit and the different responses of the circuit when the switch S is closed at time $t = 0$, with zero initial capacitor voltage and inductor current when	21
2.9	[Exercise 1] Voltage inputs applied to a resistor, capacitor, or an inductor. The units of voltage are in volts, and the time is in seconds.	22
2.10	[Exercise 2] Find the equivalent impedance of the circuit.	23
2.11	[Exercise 4]Find the equivalent impedance of the circuit.	23
2.12	[Exercise 5]Find the equivalent impedance of the circuit.	24
2.13	[Exercise 5]Find the equivalent impedance of the circuit.	24
3.1	Three most essential electronic components reviewed in this chapter.	25

Chapter 1

Contents

1. **Introduction to Rehabilitation Engineering**
2. **Fundamentals of Human Movement Mechanics**
 - What makes human movements possible?
 - Basic nerve and muscle physiology
 - Skeletal muscle mechanics
 - Sensory systems for human movement
 - Movement controller: Brain and Spinal cord
3. **Mechatronics system design process**
4. **Linear Time-Invariant Systems review**
5. **Electrical circuits review**
 - Electrical circuit elements: voltage source, current source, resistor, capacitor, inductor.
 - Electrical power and energy
 - Kirchoff's laws
 - Thevenin's and Norton's theorems
6. **Electronics review**
 - Diodes, bipolar junction transistors, Field effect transistors
 - Operational amplifiers
7. **Micrcontrollers**
 - Fundamentals

- Interfacing
- Communication protocols
- Fault detection

8. **Sensors & Signal conditioning**

- Movements sensors: potentiometer, capacitive sensor, rotary encoder, accelerometer, gyroscope, Hall effect sensor, Tachometer
- Force sensor: Strain gauge
- Proximity sensor

9. **Actuators**

- Solenoids
- Brushed DC motor
- Models of DC motor
- Brushless DC motors
- Stepper motor

10. **Automatic Control**

- Feedback systems
- Stability analysis
- PID Control
- Design of feedback control

11. **Case Studies**

- Rehabilitation robotics
- Functional electrical stimulation
- Prosthetic limbs
- Mobility aids
- Human-machine interaction

Chapter 2

Review of Basic Circuit Theory

This chapter is a quick review of basic circuit theory. Prior knowledge of these topics is assumed, along with basic understanding of linear time invariant systems - Fourier/Laplace transforms, linear constant coefficient differential equations, transfer functions, and frequency response. The reader is encouraged to review the material in this chapter before proceeding to the next chapter.

The interaction of electromagnetic fields with matters is the basis of all electrical and electronic devices. These interactions are often described, analyzed and synthesized through the abstractions of electrical circuit theory. The following are the most basic circuit two-terminal elements we will need for now. We will introduce new ones as and when they are required. Each circuit element has a unique voltage-current relationship, and it is *important* that you know these by heart.

2.1 Basic

Independent Voltage source. An Ideal voltage source provides a fixed voltage V between its two terminals, and can provide any amount of current. Notice that the voltage V can be fixed or time varying. For example, for a DC voltage source with $V = 5V$, the voltage across the two terminals will be $5V$ for all time. But for a time varying AC source, $V = 5 \sin(100\pi t)$, the voltage across its terminal will vary with time. We will often drop the adjective "independent"

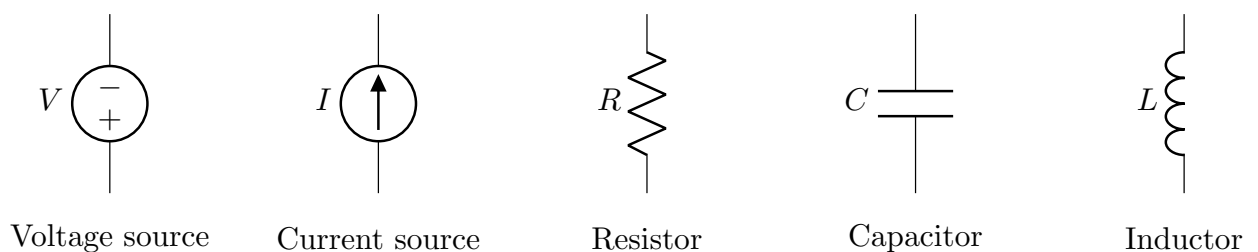


Figure 2.1: Basic circuit elements: voltage source, current source, resistor, capacitor, and inductor.

when we are sure that the context is clear. We will look at dependent sources later, and we will always use the adjective "dependent" to refer to them.

Independent Current source. An ideal current source provides a fixed amount of current to flow through its terminals (out through one and in through the other), irrespective of the voltage across its terminals. Current sources can also be time-varying.

Resistor. A passive element where the current i_R flowing through the element is proportional to the voltage v_R across its terminals.

$$v_R \propto i_R$$

In the case of linear resistors, the proportionality factor is constant, resulting in Ohm's law,

$$v_R = R i_R \quad (2.1)$$

The units of R are $V.A^{-1}$ or *Ohms* (Ω). R in general is positive. The power absorbed by a resistor is given by the product of the voltage across it and the current flowing through it,

$$P = v_R i_R = i_R^2 R = \frac{v_R^2}{R} \quad (2.2)$$

This power is dissipated as heat by the resistor. Note that the power absorbed by a resistor is always positive, since R is positive.

We will later see non-linear resistors, where the resistance varies as a function of the applied voltage, temperature and other factors.

Capacitor. A capacitor is another passive element with the following voltage current relationship.

$$i_C = C \frac{dv_C}{dt} \quad (2.3)$$

The current i_C through the capacitor is proportional to the rate of change of voltage across its terminals v_C . The proportionality factor is called the capacitance C , and has units of F (Farads) or $C \cdot V^{-1}$. The voltage across the capacitor at any given time is proportional to the integral of the current flowing through it or the charge stored in the capacitor. The voltage across the capacitor is given by

$$v_C = \frac{q}{C} = \frac{1}{C} \int i_C dt \quad (2.4)$$

The instantaneous power absorbed by the capacitor is given by,

$$P = v_C i_C = C v_C \frac{dv_C}{dt} \quad (2.5)$$

The power absorbed by the capacitor can be positive or negative, depending on the direction of current flow. If the current is flowing into the capacitor, then the voltage across it is increasing, and the power absorbed is positive. If the current is flowing out of the capacitor, then the voltage across it is decreasing, and the power absorbed is negative. A capacitor

stores energy in the form of electric field between its plates. The energy stored in a capacitor at any given time depends on the charge stored in it, and is given by,

$$E = \frac{1}{2} C v_C^2 \quad (2.6)$$

Inductor. An inductor is another passive element with the following voltage current relationship.

$$v_L = L \frac{di_L}{dt} \quad (2.7)$$

The voltage v_L across the inductor is proportional to the rate of change of current i_L flowing through it. The proportionality factor is called the inductance L , and has units of H (Henries) or $V \cdot s \cdot A^{-1}$. The current through the inductor at any given time is proportional to the integral of the voltage across it. The current through the inductor is given by

$$i_L = \frac{1}{L} \int v_L dt \quad (2.8)$$

The instantaneous power absorbed by the inductor is given by,

$$P = v_L i_L = L i_L \frac{di_L}{dt} \quad (2.9)$$

The power absorbed by the inductor can be positive or negative, depending on the direction of current flow. If the current is flowing into the inductor, then the voltage across it is increasing, and the power absorbed is positive. If the current is flowing out of the inductor, then the voltage across it is decreasing, and the power absorbed is negative. An inductor stores energy in the form of magnetic field around it. The energy stored in an inductor at any given time depends on the current flowing through it, and is given by,

$$E = \frac{1}{2} L i_L^2 \quad (2.10)$$

2.2 Kirchoff's Laws

The five elements alone are not that interesting. But interesting things can be done by connecting these elements together in different ways to form an electrical circuit. The elements are connected together by wires, which are assumed to be perfect conductors, i.e. zero resistance. Consider the following circuit (Figure 2.2),

How do we find out the voltages and currents in the circuit? Kirchoff's laws can be used for analysing such circuits, which are based on the conservation of charge and energy. The circuit in Figure 2.2 is a simple electrical circuit with a voltage source, a current source, and a bunch of resistors. The voltage source provides a fixed voltage V_s between its two terminals, and the current source provides a fixed amount of current I_s to flow through its terminals. The voltages and currents in the rest of the elements will be determined by Kirchoff's laws with the constraints imposed by the voltage and current sources. The two laws are:

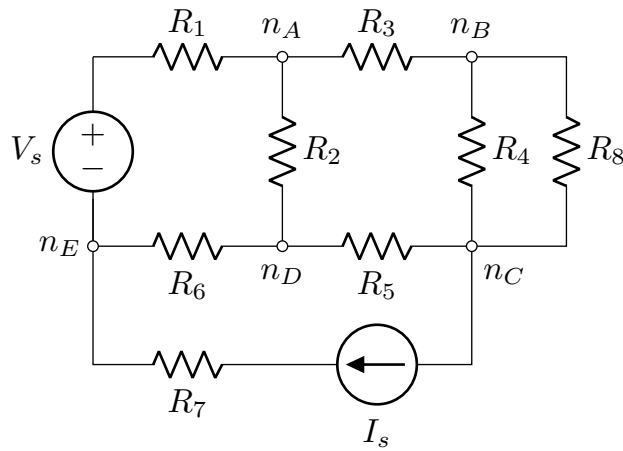


Figure 2.2: A simple electrical circuit with a voltage source, a current source, and a bunch of resistors.

1. **Kirchoff's current law (KCL):** The sum of the currents entering a node is equal to the sum of the currents leaving the node. A *node* is a point at which two or more circuit elements are connected together. In Figure 2.2, n_A , n_B , n_C , n_D and n_E are examples of nodes where three elements are connected together. There are two other nodes in the circuit, can you identify them?

The sum of the currents at a node is equal to zero. This is based on the conservation of charge, and can be expressed mathematically as:

$$\sum_{i=1}^n i_i = 0 \quad (2.11)$$

where i_i is the current flowing into or out of the node, and n is the number of elements connected to the node. The current flowing into a node is positive, and the current flowing out of a node is negative.

2. **Kirchoff's voltage law (KVL):** The sum of the voltages around a closed loop in a circuit is equal to zero. A *closed loop* is a path in the circuit that starts and ends at the same node, and does not cross itself. In Figure 2.2, the path starting from n_A , to n_D , to n_B , and back to n_A is a closed path. This path includes the resistors R_2 , R_5 , R_4 , and R_3 .

This is based on the conservation of energy, and can be expressed mathematically as:

$$\sum_{i=1}^n v_i = 0 \quad (2.12)$$

where v_i is the voltage across each element in the loop, and n is the number of elements in the loop.

The voltage across an element is positive if the current is flowing into the positive terminal of the element, and negative if the current is flowing out of the positive terminal of the element.

Note that the two laws apply for any type of circuit element used in the circuits, independent or dependent voltage/current sources, resistors, capacitors, inductors, either two, three or four terminal elements.

2.3 Series and Parallel Connections

Two elements that share the same voltage across them between a given pair of nodes are said to be **parallel** to each other. In Figure 2.2, R_4 and R_8 are parallel to each other. In a single loop, two elements that share the same current are said to be in **series** with each other. In Figure 2.2, V_s and R_1 are in series, I_s and R_7 are in series.

2.3.1 Resistors in series and parallel

When n resistors $R_1, R_2, \dots, R_n \geq 0$ are in series, these can be combined to an equivalent resistor with resistance R_{eq} given by the following,

$$R_{eq} = \sum_{i=1}^n R_i \implies R_{eq} \geq \max_{1 \leq i \leq n} R_i. \quad (2.13)$$

Note that in a series connection the equivalent resistance is at least as large as the largest value of R_1 to R_n .

When n resistors $R_1, R_2, \dots, R_n \geq 0$ are in parallel, these can be combined to an equivalent resistor with resistance R_{eq} given by the following,

$$\frac{1}{R_{eq}} = \sum_{i=1}^n \frac{1}{R_i} \implies R_{eq} = \frac{R_1 R_2 \cdots R_n}{R_1 + R_2 + \cdots + R_n} \implies R_{eq} \leq \min_{1 \leq i \leq n} R_i \quad (2.14)$$

Note that in a parallel connection, the equivalent resistance cannot be larger than the smallest value of R_1 to R_n .

2.3.2 Capacitors in series and parallel

Series connection of n capacitors $C_1, C_2, \dots, C_n \geq 0$

$$C_{eq} = \frac{C_1 C_2 \cdots C_n}{C_1 + C_2 + \cdots + C_n} \quad (2.15)$$

Parallel connection of n capacitors $C_1, C_2, \dots, C_n \geq 0$

$$C_{eq} = C_1 + C_2 + \cdots + C_n \quad (2.16)$$

2.3.3 Inductors in series and parallel

Series connection of n inductors $L_1, L_2, \dots, L_n \geq 0$

$$L_{eq} = L_1 + L_2 + \dots + L_n \quad (2.17)$$

Parallel connection of n inductors $L_1, L_2, \dots, L_n \geq 0$

$$L_{eq} = \frac{L_1 L_2 \dots L_n}{L_1 + L_2 + \dots + L_n} \quad (2.18)$$

Its left as an exercise for you to verify these expressions.

What does the equivalent resistance actually mean? The equivalent resistor with resistance R_{eq} has the same voltage-current relationship as the individual elements in series or parallel connection. We can replace the series or parallel connection of the individual resistors R_1 to R_n by a single resistor with value R_{eq} without changing the voltage current relationships in the circuit. The same argument applies for equivalent capacitors and inductors.

2.3.4 Voltage sources in series and parallel

Series connection of n voltage sources V_1, V_2, \dots, V_n will result in an equivalent voltage source V_{eq} given by

$$V_{eq} = V_1 + V_2 + \dots + V_n \quad (2.19)$$

Voltage sources should not be connected in parallel, as this will result in a short circuit. Ideally, an infinite current will flow through the connection, because the voltage sources force a potential difference between the two ends of the wire to be zero and it has zero resistance. Parallel connections are allowed only when the two sources have the same voltage and polarity.

2.3.5 Current sources in series and parallel

Parallel connection of n current sources I_1, I_2, \dots, I_n will result in an equivalent current source I_{eq} given by

$$I_{eq} = I_1 + I_2 + \dots + I_n \quad (2.20)$$

Current sources should not be connected in series; series connections are allowed only when the two sources have the same current and polarity.

2.4 Superposition Principle

Linear approximations of circuits are often employed as first order approximations when analysing circuits. A linear circuit is one that consists of linear passive elements, independent sources and linear dependent sources. Linear circuits follow the superposition principle,

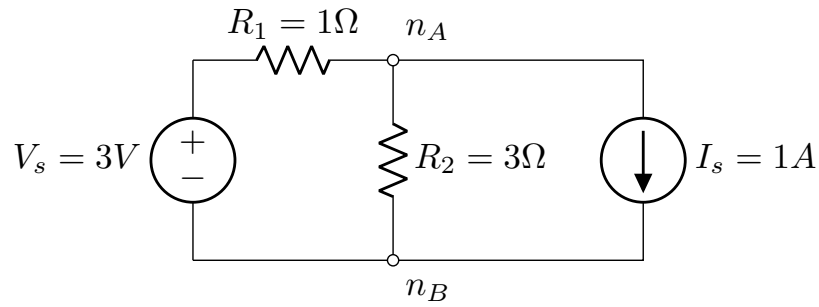


Figure 2.3: A simple circuit with two sources

which states that the response of a linear circuit to a linear combination of inputs is equal to the corresponding linear combination of the responses to each input applied separately. Solving the following circuit (Figure 2.3) should make this concept clear. For the circuit in Figure 2.3, perform the following calculation and compare your results.

Step 1. Solve for the voltage across and the current through the resistors R_1 and R_2 ; we will refer to these as v_{R1} , i_{R1} and v_{R2} , i_{R2} , respectively. You should use both Kirchoff's current and voltages laws to compute these variables.

Let's now consider of the sources in the circuit separately. This would mean making the source values “zero”. This corresponds to two different operations on the circuit. Zeroing a voltage source corresponds to replacing it with a wire (a short circuit), while zeroing a current source corresponds to simply removing the current source (an open circuit).

Step 2. Zero the voltage source V_s and compute the voltages and currents associated with the two resistors. We will refer to these as $v_{R1,V_s=0}$, $v_{R2,V_s=0}$, $i_{R1,V_s=0}$, and $i_{R2,V_s=0}$.

Step 3. Zero the current source I_s and compute the voltages and currents associated with the two resistors. We will refer to these as $v_{R1,I_s=0}$, $v_{R2,I_s=0}$, $i_{R1,I_s=0}$, and $i_{R2,I_s=0}$.

Step 4. For a linear circuit, shown in Figure 2.3, the following will always be true.

$$\begin{aligned}
 v_{R1} &= v_{R1,V_s=0} + v_{R1,I_s=0} \\
 v_{R2} &= v_{R2,V_s=0} + v_{R2,I_s=0} \\
 i_{R1} &= i_{R1,V_s=0} + i_{R1,I_s=0} \\
 i_{R2} &= i_{R2,V_s=0} + i_{R2,I_s=0}
 \end{aligned} \tag{2.21}$$

Let's assume that I am only interested in i_{R2} . Can I use $i_{R2,V_s=0}$ and $i_{R2,I_s=0}$ to compute the current i_{R2} if $V_s = 1V$ and $I_s = -2A$?

2.5 Practical Voltage and Current Sources

The independent voltage and current sources we have discussed so far are “ideal” sources. Practical or real sources do not behave like them - a battery cannot provide any amount of current for a load without any changes to the voltage across its terminals.

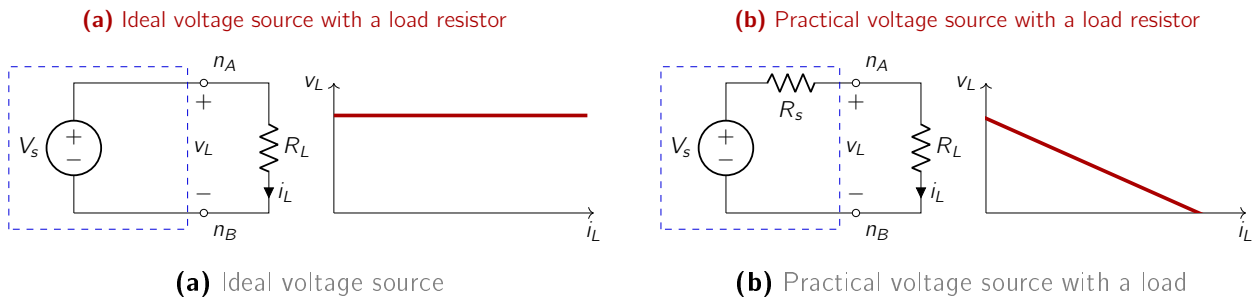


Figure 2.4: Comparison of the voltage-current relationship of an ideal and a practical voltage source.

A good model of practical voltage source is an ideal voltage source V_s in series with a *internal, source or output* resistor R_s . And for a practical current source, it is an ideal current source I_s in parallel with a resistor R_s . The voltage across the terminal of a voltage source as a function of the current drawn from it is depicted for an ideal and practical voltage source in Figure 2.4. For the ideal source (Figure 2.4a), the voltage v_L is independent of the current i_L drawn from it. For the practical voltage source (Figure 2.4b), the voltage across the terminals is a function of the current drawn from it,

$$v_L = V_s - R_s i_L \quad (2.22)$$

When $R_L = \infty$ ($i_L = 0$), the voltage across the terminals is equal to the voltage of the source V_s . This is maximum voltage the practical source can provide. This is also known as the *open circuit voltage* v_{oc} of the source. When $R_L = 0$ ($v_L = 0$), the current drawn from the source $i_L = \frac{V_s}{R_s}$. This is the maximum current the voltage source can provide. This is also known as the *short circuit current* i_{sc} of the source.

Problem 2.1. Plot the voltage-current relationship of a practical current source with $I_s = 2A$ and $R_s = 10\Omega$. What are v_{oc} and i_{sc} ?


2.6 Thevenin's and Norton's Theorems

Thevenin's and Norton's theorems are two important theorems in circuit theory that allow us to simplify complex circuits into simpler equivalent circuits. These theorems are based on the superposition principle, and can be used to analyze linear circuits with independent and dependent sources.


Thevenin's Theorem. Thevenin's theorem states that any linear circuit with independent and dependent sources can be replaced by an equivalent circuit with a single voltage source V_{th} in series with a resistor R_{th} , connected to the load resistor R_L .

Norton's Theorem. Norton's theorem states that any linear circuit with independent and dependent sources can be replaced by an equivalent circuit with a single current source I_N in parallel with a resistor R_N , connected to the load resistor R_L .

(a) Complex circuit with a load resistor

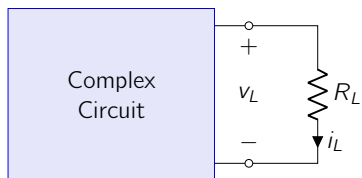

(b) Thevenin equivalent circuit

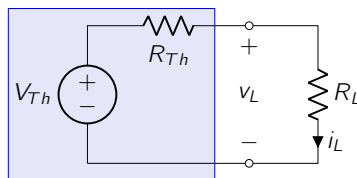

(c) Norton equivalent circuit

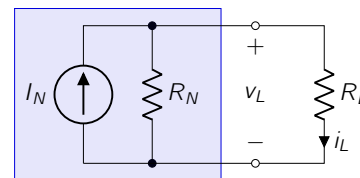


Figure 2.5: Thevenin's and Norton's circuits for a complex linear circuit. The Thevenin and Norton equivalent circuits have the same voltage-current relationship for any load.

Computing the Thevenin and Norton equivalent circuits. The Thevenin and Norton equivalent circuits can be computed using the following steps:

1. Remove the load resistor R_L from the circuit.
2. Compute the open circuit voltage v_{oc} across the terminals of the load resistor. This is the Thevenin voltage V_{th} . This can be done using the superposition principle, where we zero all the independent sources except one and compute the open circuit voltage. The overall open circuit voltage is the sum of the open circuit voltages when all other sources are zeroed.
3. Compute the short circuit current i_{sc} through the terminals of the load resistor. This is the Norton current I_N . This too can be calculated using the superposition principle.
4. Compute the Thevenin resistance R_{th} by zeroing all independent sources in the circuit and computing the equivalent resistance seen from the terminals of the load resistor (without the load resistor). This is also equal to the Norton resistance R_N .
5. The Thevenin and Norton equivalent circuits are then given by:

$$\begin{aligned} V_{th} &= v_{oc} \\ I_N &= i_{sc} \\ R_{th} &= R_N \end{aligned} \tag{2.23}$$

6. The load resistor R_L can be connected to either the Thevenin or Norton equivalent circuit, and the voltage and current across it can be computed using the voltage-current relationship of the equivalent circuit.

Problem 2.2. Compute the Thevenin and Norton equivalent circuits for the circuit shown in Fig. 2.2 assuming the following as the load resistor: (a) R_8 ; (b) R_2 ; and (c) R_7 .

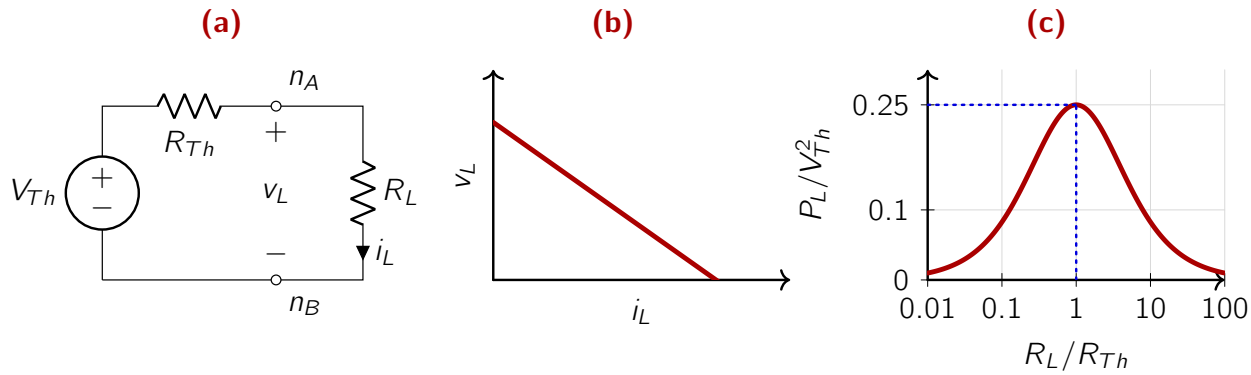


Figure 2.6: Maximum power transfer theorem.

2.7 Maximum Power Transfer Theorem

The maximum power transfer theorem states that the maximum power is transferred to the load resistor R_L when the load resistance is equal to the Thevenin resistance R_{th} of the circuit. Consider the following circuit (Figure 2.6). The power absorbed by the load resistor R_L is given by,

$$P_{R_L} = \frac{R_L}{(R_{th} + R_L)^2} V_{th}^2 \quad (2.24)$$

Its easy to check that the optimal value of R_L that maximizes the power absorbed by the load resistor is given by,

$$\begin{aligned} R_L^* &= \arg \max_{R_L} \frac{R_L}{(R_{th} + R_L)^2} V_{th}^2 = R_{Th} \\ P_L^* &= \max_{R_L} \frac{R_L}{(R_{th} + R_L)^2} V_{th}^2 = \frac{1}{4} \left(\frac{V_{Th}^2}{R_{Th}} \right) \end{aligned} \quad (2.25)$$

Problem 2.3. Prove the statements in Eq. 2.25. (*Hint:* Use the first order condition for maximization of a continuous function.)

2.8 RC, RL, and RLC Circuits

Unlike resistors, that neither remember the past values of its votlage or current, capacitors and indutors retain memory of the past current and past voltage, respectively. This can be easily seen from their respective voltage-current relationships given by Eq. 2.3 and Eq. 2.7, respectively.

Capacitor:

$$i_C = C \frac{dv_C}{dt} \implies v_C(t) = \frac{1}{C} \int_0^t i_C(\tau) d\tau + v_C(0) \quad (2.26)$$

The instantaneous voltage across a capacitor contains some information about the past history the current that has flown through the capacitor. This voltage $v_C(t)$ is determined by the charge on the capacitor at time t . Note, that the voltage across the capacitor cannot change instantaneously, as this would require an infinite current to flow through the capacitor. Theoretically, however, an impulse (Dirac delta function) current applied to the capacitor can produce instantaneous change in the capacitor's voltage.

Inductor:

$$v_L = L \frac{di_L}{dt} \implies i_L(t) = \frac{1}{L} \int_0^t v_L(\tau) d\tau + i_L(0) \quad (2.27)$$

Similarly, the instantaneous current through the inductor contains some information about the history of voltage applied across the inductor. Current through an inductor cannot change instantaneously, as this would require an infinite voltage to be applied across the inductor. An impulse voltage applied to the inductor can produce instantaneous change in the inductor's current.

RC Circuit. Consider a simple RC circuit shown in Figure 2.7a. We can write Kirchoff's voltage law for the circuit as follows,

$$RC \frac{dv_C}{dt} + v_C = V_s \implies v_C(t) = e^{-t/RC} \left[v_C(0) + \int_0^t \frac{1}{RC} e^{\tau/RC} V_s(\tau) d\tau \right] \quad (2.28)$$

The above equation gives the general solution for the voltage across the capacitor. We can derive all other variables of interest from v_C . The response to an impulse input, step input, sinusoidal input, or any arbitrary V_s can be computed using the above equation. The response for a step input obtained using a fixed sources and a switch is given in Figure 2.7a. RC is the time constant of the circuit, and is a measure of how fast the capacitor charges or discharges and it has the units of time.

Using Laplace transform to analyze the circuit, we can write the following expression for the voltage across the capacitor,


$$V_C(s) = \frac{1}{sRC + 1} V_s(s) + \frac{v_C(0)}{sRC + 1} \quad (2.29)$$

$V_C(s)$ and $V_s(s)$ are the Laplace transforms of $v_C(t)$ and $V_s(t)$. Replacing $s = j\omega$ will give us the frequency response of the system with $V_C(s)$ as the output and $V_s(s)$ as the input.

RL Circuit. Consider a simple RL circuit shown in Figure 2.7b. Kirchoff's voltage law for the circuit is as follows,



$$\frac{L}{R} \frac{di_L}{dt} + i_L = \frac{1}{R} V_s \implies i_L(t) = e^{-tR/L} \left[i_L(0) + \int_0^t \frac{1}{L} e^{\tau R/L} V_s(\tau) d\tau \right] \quad (2.30)$$

The above equation gives the general solution for the current through the inductor. The response to an impulse input, step input, sinusoidal input, or any arbitrary V_s can be computed using the above equation. The response for a step input obtained using a fixed sources and a switch is given in Figure 2.7a. $\frac{L}{R}$ is the time constant of the circuit, and is a measure of how fast the current through the inductor can change; it has the units of time.

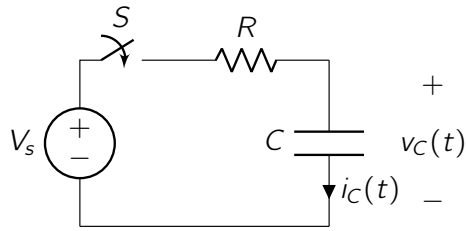(a) A Simple RC Circuit


Assuming the switch S is closed at $t = 0$, the voltage across the capacitor $v_C(t)$ is given by,

$$v_C(t) = V_s \cdot \left(1 - e^{-\frac{t}{RC}}\right) + v_C(0)e^{-\frac{t}{RC}}, \quad t \geq 0$$

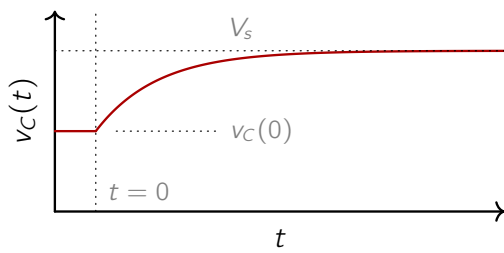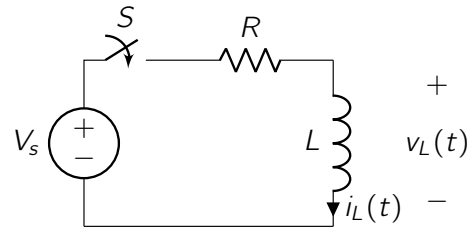**(a)** Ideal voltage source**(b) A Simple RL Circuit**

Assuming the switch S is closed at $t = 0$, the current through the inductor $i_L(t)$ is given by,

$$i_L(t) = \frac{V_s}{R} \cdot \left(1 - e^{-\frac{t}{L/R}}\right) + i_L(0)e^{-\frac{t}{L/R}}, \quad t \geq 0$$

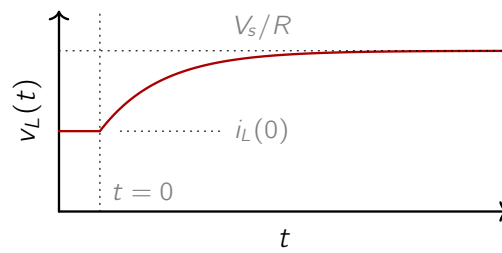**(b)** Practical voltage source with a load**Figure 2.7:** Simple RC and RL circuits and their transient responses.

Similarly, applying the Laplace transform, we have,

$$I_L(s) = \frac{1}{sL + R}V_s(s) + \frac{i_L(0)}{sL + R} \quad (2.31)$$

RLC Circuit. Consider a simple series RLC circuit shown in Figure 2.8. Kirchhoff's voltage law for the circuit is as follows,


$$LC \frac{d^2 v_C}{dt^2} + RC \frac{dv_C}{dt} + v_C = V_s \quad (2.32)$$

The response of the circuit when the switch is closed at $t = 0$ is qualitatively different depending on the values of R , L and C . This is better understood in the Laplace domain. The Laplace transform of the response $v_C(t)$ is given by,

$$V_C(s) = \frac{V_s(s)}{LCs^2 + RCs + 1} + v_C(0) \frac{C(Ls + R)}{LCs^2 + RCs + 1} + i_L(0) \frac{RC}{LCs^2 + RCs + 1} \quad (2.33)$$

Note that $i_L(0) = \frac{dv_C}{dt}(0)$. The denominator of the above equation is a second order polynomial in s , and thus the response of the circuit will depend on the roots of the polynomial. The four different responses are shown in Figure 2.8.

(a) A Simple RLC Circuit

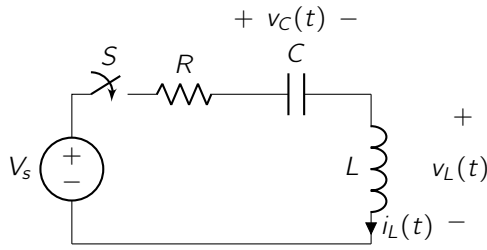

(b) Four different step responses

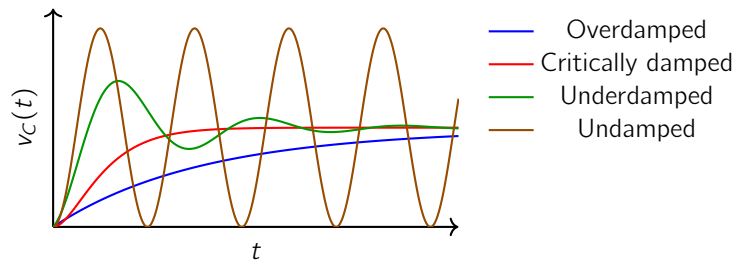


Figure 2.8: A simple RLC circuit and the different responses of the circuit when the switch S is closed at time $t = 0$, with zero initial capacitor voltage and inductor current when $t = 0$.

2.9 Steady State Sinusoidal Analysis

The previous subsection looked at the transient response of the some simple circuits involving R , L , and C . However, we are often interested in the steady state response of these circuits to sinusoidal excitations. This is because sinusoidal signals are eigenfunctions of linear systems, such as the linear circuits we have discussed so far. With sinusoidal excitations, all currents and voltages in the circuit will also be sinusoidal with the same frequency as the input excitations, although with different amplitudes and phases. Complex numbers are used in this analysis for compact representation of amplitude and phase of signals.

For steady state frequency analysis for circuits involving R , L , and C , we extend the idea of resistance to impedance. Fourier transforms provide a natural way to analyze the steady state response of linear circuits to sinusoidal excitations. We first recast the voltage-current relationships of the circuit elements in the Fourier domain.

$$\begin{aligned}
 \text{Resistor: } v_R &= R i_R \implies V_R(j\omega) = R \cdot I_R(j\omega) \\
 \text{Capacitor: } i_C &= C \frac{dv_C}{dt} \implies V_C(j\omega) = \frac{1}{j\omega C} \cdot I_C(j\omega) \\
 \text{Inductor: } v_L &= L \frac{di_L}{dt} \implies V_L(j\omega) = j\omega L \cdot I_L(j\omega)
 \end{aligned} \tag{2.34}$$

The Fourier transformed voltage-current relationships of the circuit elements look like Ohms law, with the concept of resistance extended to impedance. The impedance of a capacitor and inductor defined as the ratio of the Fourier transformed voltage to the Fourier transformed current. They are functions of the frequency of the voltage/current. The impedance of a resistor, capacitor, and inductor are given by,

$$\begin{aligned}
 \text{Resistor: } Z_R &= R \\
 \text{Capacitor: } Z_C &= \frac{1}{j\omega C} \\
 \text{Inductor: } Z_L &= j\omega L
 \end{aligned} \tag{2.35}$$

Equivalent Impedance. The equivalent impedance of a circuit with impedances Z_1, Z_2, \dots, Z_n in series is given by $Z_{eq} = Z_1 + Z_2 + \dots + Z_n$. When the impedances Z_1, Z_2, \dots, Z_n are in parallel, the equivalent impedances is given by $\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n}$.

Amplitude and phase modification by an impedance. If a sinusoidal current excitation $i(t) = I_o \sin(\omega t)$ is passed through an impedance Z . Then the voltage across the impedance is given by,

$$v(t) = |Z|I_o \sin(\omega t + \arg Z) \quad (2.36)$$

The amplitude of the sinusoidal voltage is $|Z|I_o$, and the phase of the sinusoidal voltage is $\arg Z$, with respect to the current $i(t)$.

2.10 Exercise

- Plot the current through a resistor $R = 10\Omega$, capacitor $C = 5\mu F$, and inductor $L = 2mH$ for the following voltage inputs.

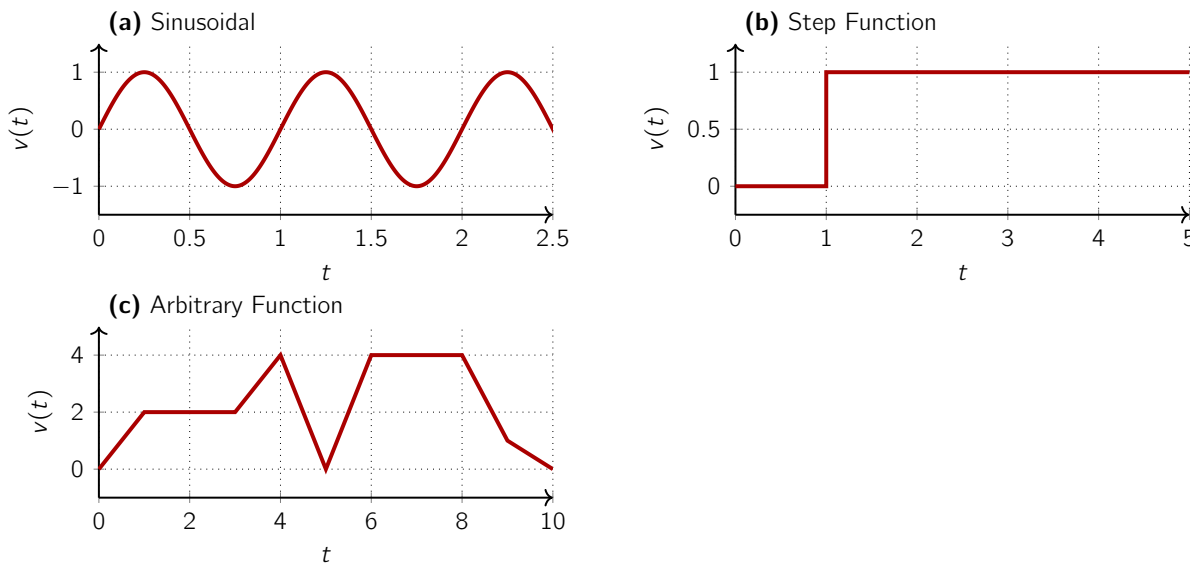


Figure 2.9: [Exercise 1] Voltage inputs applied to a resistor, capacitor, or an inductor. The units of voltage are in volts, and the time is in seconds.

- Find the Thevenin and Norton equivalent circuits of the following circuits (Figure 2.10). Note that one of the problems has a dependent source. Dependent sources are voltage or current sources (diamond shaped elements), whose voltage or current, respectively, depend on the voltage or current across another element in the circuit.
- A certain red LED has a maximum current rating of $35mA$, and if this value is exceeded, overheating and catastrophic failure will result. The resistance of the LED is a nonlinear

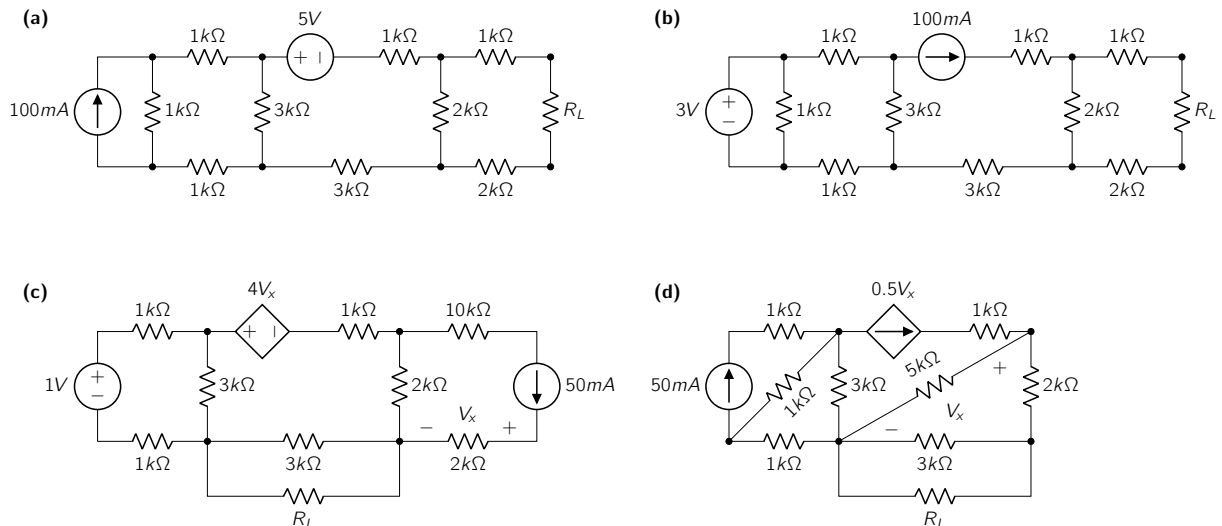


Figure 2.10: [Exercise 2] Find the equivalent impedance of the circuit.

function of its current, but the manufacturer warrants a minimum resistance of 47Ω and a maximum resistance of 117Ω . Only 9V batteries are available to power the LED. Design a suitable circuit to deliver the maximum power possible to the LED without damaging it. Use only combinations of the standard resistor values. (*This problem is from Engineering Circuit Analysis by Hayt Jr. et al.*)

4. The load resistor in Figure 2.11 can safely dissipate up to 1W before overheating and bursting into flame. The lamp can be treated as a 10.6Ω resistor if less than 1A flows through it and a 15Ω resistor if more than 1A flows through it. What is the maximum permissible value of I_s ? Verify your answer with an appropriate computer simulation. (*This problem is from Engineering Circuit Analysis by Hayt Jr. et al.*)

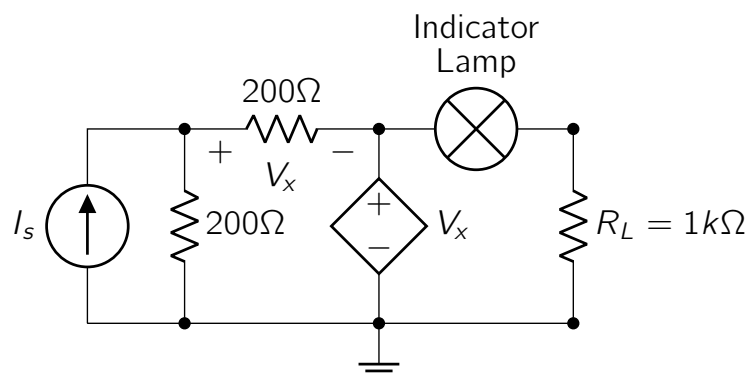


Figure 2.11: [Exercise 4] Find the equivalent impedance of the circuit.

5. In the following circuit (Figure 2.12), find the voltage across the capacitors C_1 and C_2 .

The single pole double throw switch S is connected to the top terminal before time $t = 0$. At time $t = 0$, switch is flipped to the bottom terminal. Assume that before time $t = 0$, the voltage across the capacitor C_2 , $v_{C2} = 1V$. Draw the plot of the voltage across the capacitors C_1 and C_2 as function of time.

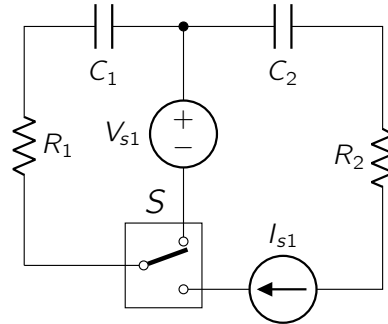


Figure 2.12: [Exercise 5] Find the equivalent impedance of the circuit.

6. Figure 2.13 shows a voltage divider circuit with a sinusoidal voltage source $V_s(t) = 10 \sin(1000\pi t)$. The impedance $Z_1 = 3 + j4\Omega$. What should the impedance Z_2 be if the voltage across Z_2 has one-fourth the amplitude of V_s and with a phase difference of 45° ?

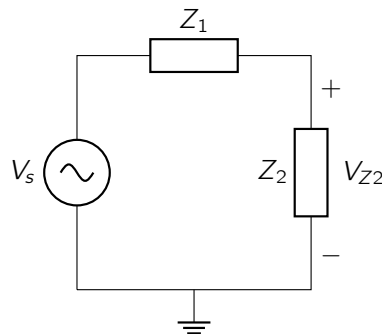


Figure 2.13: [Exercise 5] Find the equivalent impedance of the circuit.

Chapter 3

Electronics Review

This chapter is a quick review of basic electronics. The previous chapter involved simple, linear passive two terminal elements, which are essential for building most electrical circuits. This chapter will focus on some essential non-linear, two/three terminal electronics components which form the basis for more useful electronics circuits such as amplifiers, oscillators, filters, power supplies, switches, etc. We will review three important electronic components and their circuits in this chapter: *diode*, *bipolar junction transistor (BJT)*, and *metal oxide field effect transistor*.

3.1 Basic semiconductor concepts

Conductivity of a material is proportional the concentration of free electrons.

$$\begin{aligned}\textbf{Conductor: } n_{cond} &\approx 10^{28} \text{electrons}/\text{m}^3 \\ \textbf{Insulator: } n_{ins} &\approx 10^7 \text{electrons}/\text{m}^3 \\ \textbf{Semiconductor: } n_{ins} &< n_{sem} < n_{cond}\end{aligned}\tag{3.1}$$

3.1.1 Intrinsic semiconductors

Silicon or Germanium have crystalline structure with four covalent bonds between neighbouring atoms. At $0^\circ K$ semiconductors all covalent bonds are in place tightly holding on to electrons

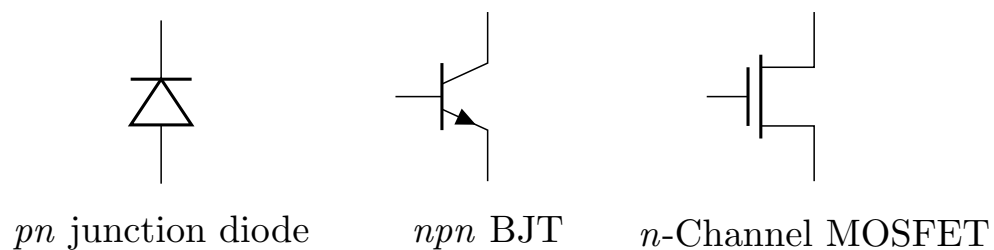


Figure 3.1: Three most essential electronic components reviewed in this chapter.

in the bonds. Thus these behave as perfect insulators at low temperatures. With increase in temperature, covalent bonds are ruptured, releasing *free electrons* to roam around in the crystal and become available for conduction when there is an externally applied electric field. The missing electron in the ruptured covalent bond is called a hole, which too act as carrier of electricity. When an electric field is applied, electrons from neighbouring covalent bonds jump into a hole creating a hole in their previous bond. This results in the hole effectively moving the direction opposite to the jumping electrons from the covalent bonds. Thus, unlike conductors, semiconductors can have two types of charge carriers: *electrons* and *holes*. The concentration of free electrons and holes in a semiconductor determines its conductivity, which is controlled by temperature. In intrinsic semiconductors, the concentration of free electrons and holes is equal, i.e. $n_{e^-} = n_{h^+} = n_i$. This concentration is given by,

$$n_i = B T^{3/2} e^{-\frac{E_g}{k_B T}} \quad (3.2)$$

where B is a material constant ($7.3 \times 10^{15} \text{cm}^{-3} \text{K}^{-3/2}$ for Si), E_g is the band gap energy, k_B is the Boltzmann constant, and T is the absolute temperature in Kelvin. The band gap energy is the energy required to break a covalent bond and create a free electron-hole pair. It should be noted that the conductivity of semiconductors increases with temperature, making them suitable for thermometry.

3.1.2 Doped Semiconductors

With intrinsic semiconductors, the conductivity is still quite small at room temperature. Another precise and controlled way to change a semiconductor's conductivity is by adding impurities, called *doping*. The two types of doping are: ***n-type*** and ***p-type*** doping. In ***n-type*** doping, a small amount of pentavalent atoms (e.g. Phosphorus, Arsenic) are added to the semiconductor. These atoms have five valence electrons, and when added to the silicon crystal, four of these electrons form covalent bonds with the neighbouring silicon atoms, while the fifth electron is free to roam around in the crystal. This results in an increase in the concentration of free electrons, making the semiconductor more conductive. The concentration of free electrons in an ***n-type*** semiconductor is given by,

$$n_{e^-} = n_i + N_D \quad n_{h^+} = n_i \quad (3.3)$$

3.2 Diode