

# **Mechatronics for Rehabilitation Engineering: Course Notes**

Sivakumar Balasubramanian  
CMC Vellore

Update on May 21, 2025



# Contents

<b>1</b>	<b>Contents</b>	<b>7</b>
<b>2</b>	<b>Electronics Review</b>	<b>9</b>

2.1	Review of Basic Circuit Theory	9
2.1.1	Kirchoff's Laws . . . . .	11
2.1.2	Series and Parallel Connections . . . . .	13
2.1.3	Superposition Principle	14
2.1.4	Practical Voltage and Current Sources . . . . .	15
2.1.5	Thevenin's and Nor- ton's Theorems . . . . .	16
2.1.6	Maximum Power Transfer Theorem . . . . .	17



# List of Figures

2.1	Basic circuit elements: voltage source, current source, resistor, capacitor, and inductor. . . . .	9
2.2	A simple electrical circuit with a voltage source, a current source, and a bunch of resistors. . . . .	12
2.3	A simple circuit with two sources . . . . .	15
2.4	Comparison of the voltage-current relationship of an ideal and a practical voltage source. . . . .	16
2.5	Thevenin's and Norton's circuits for a complex linear circuit. The Thevenin and Norton equivalent circuits have the same voltage-current relationship for any load. . . . .	17
2.6	Maximum power transfer theorem. . . . .	18



# Chapter 1

## Contents

1. **Introduction to Rehabilitation Engineering**
2. **Fundamentals of Human Movement Mechanics**
  - What makes human movements possible?
  - Basic nerve and muscle physiology
  - Skeletal muscle mechanics
  - Sensory systems for human movement
  - Movement controller: Brain and Spinal cord
3. **Mechatronics system design process**
4. **Linear Time-Invariant Systems review**
5. **Electrical circuits review**
  - Electrical circuit elements: voltage source, current source, resistor, capacitor, inductor.
  - Electrical power and energy
  - Kirchoff's laws
  - Thevenin's and Norton's theorems
6. **Electronics review**
  - Diodes, bipolar junction transistors, Field effect transistors
  - Operational amplifiers
7. **Micrcontrollers**
  - Fundamentals

- Interfacing
- Communication protocols
- Fault detection

### 8. **Sensors & Signal conditioning**

- Movements sensors: potentiometer, capacitive sensor, rotary encoder, accelerometer, gyroscope, Hall effect sensor, Tachometer
- Force sensor: Straining gauge
- Proximity sensor

### 9. **Actuators**

- Solenoids
- Brushed DC motor
- Models of DC motor
- Brushless DC motors
- Stepper motor

### 10. **Automatic Control**

- Feedback systems
- Stability analysis
- PID Control
- Design of feedback control

### 11. **Case Studies**

- Rehabilitation robotics
- Functional electrical stimulation
- Prosthetic limbs
- Mobility aids
- Human-machine interaction



# Chapter 2


## Electronics Review

This chapter is a quick review of basic circuit theory and electronics. Prior knowledge of these topics is assumed, along with basic understanding of linear time invariant systems - Fourier/Laplace transforms, linear constant coefficient differential equations, transfer functions, and frequency response. The reader is encouraged to review the material in this chapter before proceeding to the next chapter.

### 2.1 Review of Basic Circuit Theory

The interaction of electromagnetic fields with matters is the basis of all electrical and electronic devices. These interactions are often described, analyzed and synthesized through the abstractions of electrical circuit theory. The following are the most basic circuit two-terminal elements we will need for now. We will introduce new ones as and when they are required. Each circuit element has a unique voltage-current relationship, and it is *important* that you know these by heart.

**Independent Voltage source.** An idea voltage source provides a fixed voltage  $V$  between its two terminals, and can provide any amount of current. Notice that the voltage  $V$  can be fixed or time varying. For example, for a DC vortlage source with  $V = 5V$ , the voltage across the two terminals will be  $5V$  for all time. But for a time varying AC source,  $V = 5 \sin(100\pi t)$ , the voltage across its terminal will vary with time. We will often drop the adjective "independent"

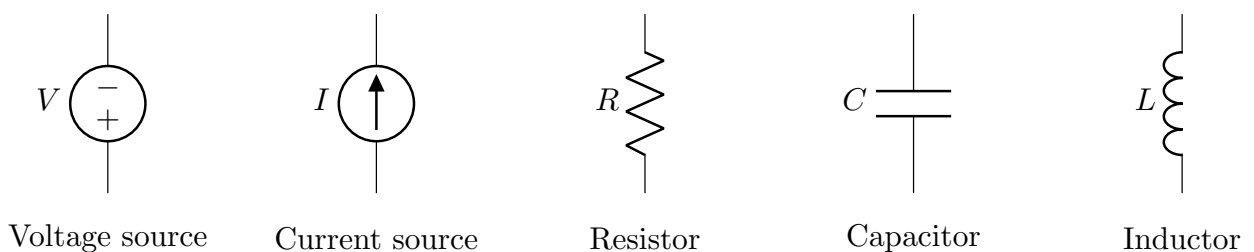

**Figure 2.1:** Basic circuit elements: voltage source, current source, resistor, capacitor, and inductor.

when we are sure that the context is clear. We will look at dependent sources later, and we will always use the adjective "dependent" to refer to them.

**Independent Current source.** An ideal current source provides a fixed amount of current to flow through its terminals (out through one and in through the other), irrespective of the voltage across its terminals. Current sources can also be time-varying.

**Resistor.** A passive element where the current  $i_R$  flowing through the element is proportional to the voltage  $v_R$  across its terminals.

$$v_R \propto i_R$$

In the case of linear resistors, the proportionality factor is constant, resulting in Ohm's law,

$$v_R = R i_R \quad (2.1)$$

The units of  $R$  are  $V \cdot A^{-1}$  or *Ohms* ( $\Omega$ ).  $R$  is in general positive. The power absorbed by a resistor is given by the product of the voltage across it and the current flowing through the resistor,

$$P = v_R i_R = i_R^2 R = \frac{v_R^2}{R} \quad (2.2)$$

This power is dissipated as heat by the resistor. Note that the power absorbed by a resistor is always positive, since  $R$  is positive.

We will later see non-linear resistors, where the resistance varies as a function of the applied voltage, temperature and other factors.

**Capacitor.** A capacitor is another passive element with the following voltage current relationship.

$$i_C = C \frac{dv_C}{dt} \quad (2.3)$$

The current  $i_C$  through the capacitor is proportional to the rate of change of voltage across its terminals  $v_C$ . The proportionality factor is called the capacitance  $C$ , and has units of  $F$  (Farads) or  $C \cdot V^{-1}$ . The voltage across the capacitor is given by at any given time is proportional to the integral of the current flowing through it or the charge stored in the capacitor. The voltage across the capacitor is given by

$$q = C v_C \quad (2.4)$$

The instantaneous power absorbed by the capacitor is given by,

$$P = v_C i_C = C v_C \frac{dv_C}{dt} \quad (2.5)$$

The power absorbed by the capacitor can be positive or negative, depending on the direction of current flow. If the current is flowing into the capacitor, then the voltage across it is increasing, and the power absorbed is positive. If the current is flowing out of the capacitor, then the voltage across it is decreasing, and the power absorbed is negative. A capacitor

stores energy in the electric field between its plates. The energy stored in a capacitance at any given time depends on the charge stored in it, and is given by,

$$E = \frac{1}{2} C v_C^2 \quad (2.6)$$

**Inductor.** An inductor is another passive element with the following voltage current relationship.

$$v_L = L \frac{di_L}{dt} \quad (2.7)$$

The voltage  $v_L$  across the inductor is proportional to the rate of change of current  $i_L$  flowing through it. The proportionality factor is called the inductance  $L$ , and has units of  $H$  (Henries) or  $V \cdot s \cdot A^{-1}$ . The current through the inductor is given by at any given time is proportional to the integral of the voltage across it. The current through the inductor is given by

$$i_L = \frac{1}{L} \int v_L dt \quad (2.8)$$

The instantaneous power absorbed by the inductor is given by,

$$P = v_L i_L = L i_L \frac{di_L}{dt} \quad (2.9)$$


The power absorbed by the inductor can be positive or negative, depending on the direction of current flow. If the current is flowing into the inductor, then the voltage across it is increasing, and the power absorbed is positive. If the current is flowing out of the inductor, then the voltage across it is decreasing, and the power absorbed is negative. An inductor stores energy in the magnetic field around it. The energy stored in an inductor at any given time depends on the current flowing through it, and is given by,

$$E = \frac{1}{2} L i_L^2 \quad (2.10)$$

### 2.1.1 Kirchoff's Laws

The five elements alone are not that interesting. But interesting things can be done by connecting these elements together in different ways to form an electrical circuit. The elements are connected together by wires, which are assumed to be perfect conductors, i.e. zero resistance. Consider the following circuit (Figure 2.1),

How do we find out the voltages and currents in the circuit? Kirchoff's laws can be used for analysing such circuits, which are based on the conservation of charge and energy. The circuit in Figure 2.2 is a simple electrical circuit with a voltage source, a current source, and a bunch of resistors. The voltage source provides a fixed voltage  $V_s$  between its two terminals, and the current source provides a fixed amount of current  $I_s$  to flow through its terminals. The voltages and currents in the rest of the elements will be determined by Kirchoff's laws with the constraints imposed by the voltage and current sources. The two laws are:

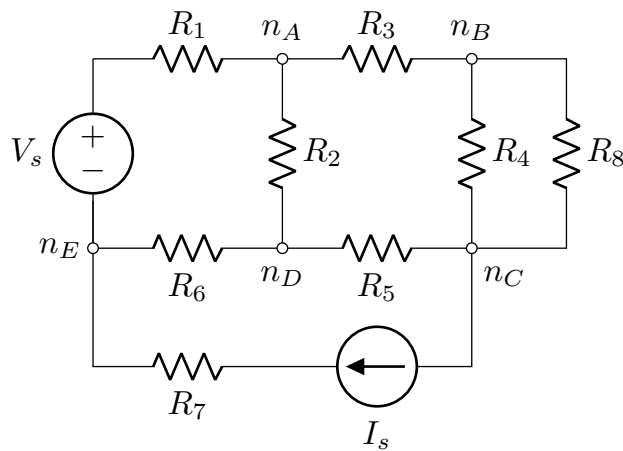

**Figure 2.2:** A simple electrical circuit with a voltage source, a current source, and a bunch of resistors.

1. **Kirchoff's current law (KCL):** The sum of the currents entering a node is equal to the sum of the currents leaving the node. A *node* is a point at which two or more circuit elements are connected together. In Figure 2.2,  $n_A$ ,  $n_B$ ,  $n_C$  and  $n_D$  are examples of nodes where three elements are connected together. There are three other nodes in the circuit, can you identify them?

The sum of the currents at a node is equal to zero. This is based on the conservation of charge, and can be expressed mathematically as:

$$\sum_{i=1}^n i_i = 0 \quad (2.11)$$

where  $i_i$  is the current flowing into or out of the node, and  $n$  is the number of elements connected to the node. The current flowing into a node is positive, and the current flowing out of a node is negative.

2. **Kirchoff's voltage law (KVL):** The sum of the voltages around a closed loop in a circuit is equal to zero. A *closed loop* is a path in the circuit that starts and ends at the same node, and does not cross itself. In Figure 2.2, the path starting from  $n_A$ , to  $n_D$ , to  $n_B$ , and back to  $n_A$  is a closed path. This path includes the resistors  $R_3$ ,  $R_4$ ,  $R_5$ , and  $R_2$ .

This is based on the conservation of energy, and can be expressed mathematically as:

$$\sum_{i=1}^n v_i = 0 \quad (2.12)$$

where  $v_i$  is the voltage across each element in the loop, and  $n$  is the number of elements in the loop.

The voltage across an element is positive if the current is flowing into the positive terminal of the element, and negative if the current is flowing out of the positive terminal of the element.

Note that the two laws apply for any type of circuit element used in the circuits, independent or dependent voltage/current sources, resistors, capacitors, inductors, other two, three or four terminal elements.

### 2.1.2 Series and Parallel Connections

Two elements that share the same voltage across them between a given pair of nodes are said to be **parallel** to each other. In Figure 2.2,  $R_4$  and  $R_8$  are parallel to each other. In a single loop, two elements that share the same current are said to be in **series** with each other. In Figure 2.2,  $V_s$  and  $R_1$  are in series,  $I_s$  and  $R_7$  are in series.

#### Resistors in series and parallel

When  $n$  resistors  $R_1, R_2, \dots, R_n \geq 0$  are in series, these can be combined to an equivalent resistor with resistance  $R_{eq}$  given by the following,

$$R_{eq} = \sum_{i=1}^n R_i \implies R_{eq} \geq \max_{1 \leq i \leq n} R_i. \quad (2.13)$$

Note that in a series connection the equivalent resistance is at least as large as the largest value of  $R_1$  to  $R_n$ .

When  $n$  resistors  $R_1, R_2, \dots, R_n \geq 0$  are in parallel, these can be combined to an equivalent resistor with resistance  $R_{eq}$  given by the following,

$$\frac{1}{R_{eq}} = \sum_{i=1}^n \frac{1}{R_i} \implies R_{eq} = \frac{R_1 R_2 \dots R_n}{R_1 + R_2 + \dots + R_n} \implies R_{eq} \leq \min_{1 \leq i \leq n} R_i \quad (2.14)$$

Note that in a parallel connection, the equivalent resistance cannot be larger than the smallest value of  $R_1$  to  $R_n$ .

#### Capacitors in series and parallel

**Series connection** of  $n$  capacitors  $C_1, C_2, \dots, C_n \geq 0$

$$C_{eq} = \frac{C_1 C_2 \dots C_n}{C_1 + C_2 + \dots + C_n} \quad (2.15)$$

**Parallel connection** of  $n$  capacitors  $C_1, C_2, \dots, C_n \geq 0$

$$C_{eq} = C_1 + C_2 + \dots + C_n \quad (2.16)$$

### Inductors in series and parallel

**Series connection** of  $n$  capacitors  $L_1, L_2, \dots, L_n \geq 0$

$$L_{eq} = L_1 + L_2 + \dots + L_n \quad (2.17)$$

**Parallel connection** of  $n$  capacitors  $L_1, L_2, \dots, L_n \geq 0$

$$L_{eq} = \frac{L_1 L_2 \dots L_n}{L_1 + L_2 + \dots + L_n} \quad (2.18)$$

Its left as an exercise for you to verify these expressions.

**What does the equivalent resistance actually mean?** The equivalent resistor with resistance  $R_{eq}$  has the same voltage-current relationship as the individual elements in series or parallel connection. We can replace the series or parallel connection of the individual resistors  $R_1$  to  $R_n$  by a single resistor with value  $R_{eq}$  without changing the voltage current relationships in the circuit. The same argument applies for equivalent capacitors and inductors.

### Voltage sources in series and parallel

**Series connection** of  $n$  voltage sources  $V_1, V_2, \dots, V_n$  will result in an equivalent voltage source  $V_{eq}$  given by

$$V_{eq} = V_1 + V_2 + \dots + V_n \quad (2.19)$$

Voltage sources should not be connected in parallel, as this will result in a short circuit. Ideally, an infinite current will flow through the connection, because the voltage sources force a potential difference between the two end of the wires and it has zero resistance. Parallel connections are allowed only when the two sources have the same voltage and polarity.

### Current sources in series and parallel


**Parallel connection** of  $n$  current sources  $I_1, I_2, \dots, I_n$  will result in an equivalent current source  $I_{eq}$  given by

$$I_{eq} = I_1 + I_2 + \dots + I_n \quad (2.20)$$

Current sources should not be connected in series; series connections are allowed only when the two sources have the same current and polarity.

## 2.1.3 Superposition Principle

Linear approximations of circuits are often employed as first order approximations when analysing circuits. A linear circuit is one that consists of linear passive elements, independent sources and linear dependent sources. Linear circuits follow the superposition principle, which states that the response of a linear circuit to a linear combination of inputs is equal to the corresponding linear combination of the responses to each input applied separately.

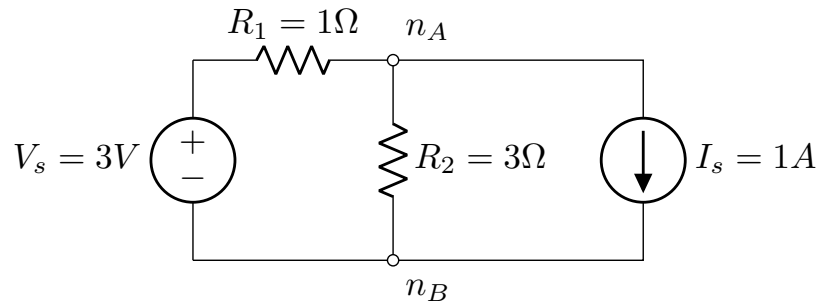

**Figure 2.3:** A simple circuit with two sources

Solving the following circuit (Figure 2.3) should make this concept clear. For the circuit in Figure 2.3, perform the following calculation and compare your results.

**Step 1.** Solve for the voltage across and the current through the resistors  $R_1$  and  $R_2$ ; we will refer to these as  $v_{R1}$ ,  $i_{R1}$  and  $v_{R2}$ ,  $i_{R2}$ , respectively. You should use both Kirchoff's current and voltages laws to compute these variables.

Let's now consider of the sources in the circuit separately. This would mean making the source values "zero". This corresponds to two different operations on the circuit. Zeroing a voltage source corresponds to replacing it with a wire (a short circuit), while zeroing a current source corresponds to simply removing the current source (an open circuit).

**Step 2.** Zero the voltage source  $V_s$  and compute the voltages and currents associated with the two resistors. We will refer to these as  $v_{R1,V_s=0}$ ,  $v_{R2,V_s=0}$ ,  $i_{R1,V_s=0}$ , and  $i_{R2,V_s=0}$ .

**Step 3.** Zero the current source  $I_s$  and compute the voltages and currents associated with the two resistors. We will refer to these as  $v_{R1,I_s=0}$ ,  $v_{R2,I_s=0}$ ,  $i_{R1,I_s=0}$ , and  $i_{R2,I_s=0}$ .

**Step 4.** For a linear circuit, shown in Figure 2.3, the following will always be true.


$$\begin{aligned}
 v_{R1} &= v_{R1,V_s=0} + v_{R1,I_s=0} \\
 v_{R2} &= v_{R2,V_s=0} + v_{R2,I_s=0} \\
 i_{R1} &= i_{R1,i_s=0} + i_{R1,I_s=0} \\
 i_{R2} &= i_{R2,i_s=0} + i_{R2,I_s=0}
 \end{aligned} \tag{2.21}$$

Let's assume that I am only interested in  $i_{R2}$ . Can I use  $i_{R2,V_s=0}$  and  $i_{R2,I_s=0}$  to compute the current  $i_{R2}$  if  $V_s = 1V$  and  $I_s = -2A$ ?

### 2.1.4 Practical Voltage and Current Sources

The independent voltage and current sources we have discussed so far are "ideal" sources. Practical or real sources do not behave like them - a battery cannot provide any amount of current for a load without any changes to the voltage across its terminals.

A good model of practical voltage source is an ideal voltage source  $V_s$  in series with a *internal, source or output* resistor  $R_s$ . And for a practical current source, it is an ideal current source  $I_s$  in parallel with a resistor  $R_s$ . The voltage across the terminal of a voltage source

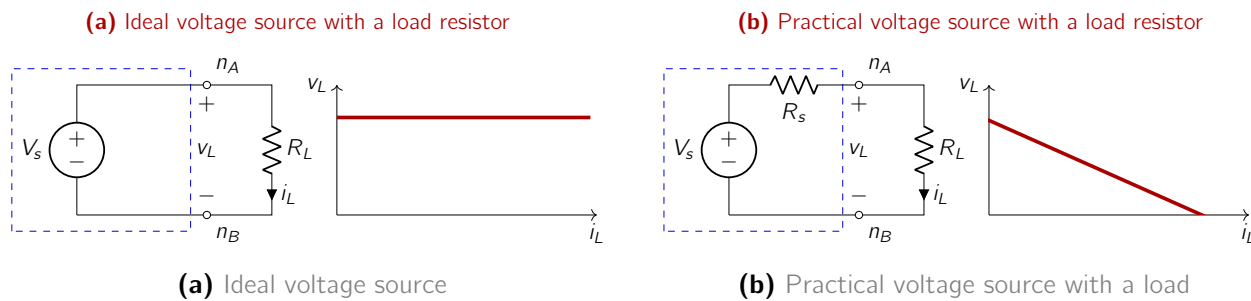

**Figure 2.4:** Comparison of the voltage-current relationship of an ideal and a practical voltage source.

as function of the current draw from it is depicted for an ideal and practical voltage source in Figure 2.4. For the ideal source (Figure 2.4a), the voltage  $v_L$  is independent of the current  $i_L$  drawn from it. For the practical voltage source (Figure 2.4b), the voltage across the terminals is a function of the current drawn from it,

$$v_L = V_s - R_s i_L \quad (2.22)$$

When  $R_L = \infty$  ( $i_L = 0$ ), the voltage across the terminals is equal to the voltage of the source  $V_s$ . This is maximum voltage the practical source can provide. This is also known as the *open circuit voltage*  $v_{oc}$  of the source. When  $R_L = 0$  ( $v_L = 0$ ), the current drawn from the source  $i_L = \frac{V_s}{R_s}$ . This is the maximum current the voltage source can provide. This is also known as the *short circuit current*  $i_{sc}$  of the source.

**Problem 2.1.** Plot the voltage-current relationship of a practical current source with  $I_s = 2A$  and  $R_s = 10\Omega$ . What are  $v_{oc}$  and  $i_{sc}$ ?

### 2.1.5 Thevenin's and Norton's Theorems

Thevenin's and Norton's theorems are two important theorems in circuit theory that allow us to simplify complex circuits into simpler equivalent circuits. These theorems are based on the superposition principle, and can be used to analyze linear circuits with independent and dependent sources.

**Thevenin's Theorem.** Thevenin's theorem states that any linear circuit with independent and dependent sources can be replaced by an equivalent circuit with a single voltage source  $V_{th}$  in series with a resistor  $R_{th}$ , connected to the load resistor  $R_L$ .


**Norton's Theorem.** Norton's theorem states that any linear circuit with independent and dependent sources can be replaced by an equivalent circuit with a single current source  $I_N$  in parallel with a resistor  $R_N$ , connected to the load resistor  $R_L$ .

**Computing the Thevenin and Norton equivalent circuits.** The Thevenin and Norton equivalent circuits can be computed using the following steps:


1. Remove the load resistor  $R_L$  from the circuit.




(a) Complex circuit with a load resistor

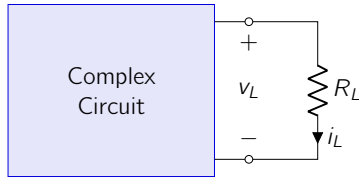

(b) Thevenin equivalent circuit

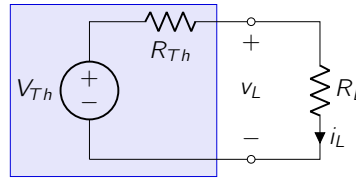

(c) Norton equivalent circuit

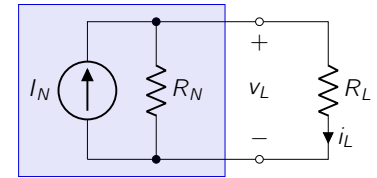

**Figure 2.5:** Thevenin's and Norton's circuits for a complex linear circuit. The Thevenin and Norton equivalent circuits have the same voltage-current relationship for any load.

2. Compute the open circuit voltage  $v_{oc}$  across the terminals of the load resistor. This is the Thevenin voltage  $V_{th}$ . This can be using the superposition principle, where we zero all the independent sources except one and compute the open circuit voltage. The overall open circuit voltage is the sum of the open circuit voltages when all other sources are zeroed.
3. Compute the short circuit current  $i_{sc}$  through the terminals of the load resistor. This is the Norton current  $I_N$ . This too can be calculated using the superposition principle.
4. Compute the Thevenin resistance  $R_{th}$  by zeroing all independent sources in the circuit and computing the equivalent resistance seen from the terminals of the load resistor (without the load resistor). This is also equal to the Norton resistance  $R_N$ .
5. The Thevenin and Norton equivalent circuits are then given by:


$$\begin{aligned} V_{th} &= v_{oc} \\ I_N &= i_{sc} \\ R_{th} &= R_N \end{aligned} \tag{2.23}$$

6. The load resistor  $R_L$  can be connected to either the Thevenin or Norton equivalent circuit, and the voltage and current across it can be computed using the voltage-current relationship of the equivalent circuit.

**Problem 2.2.** Compute the Thevenin and Norton equivalent circuits for the circuit shown in Fig. 2.2 assuming the following as the load resistor: (a)  $R_8$ ; (b)  $R_2$ ; and (c)  $R_7$ .

### 2.1.6 Maximum Power Transfer Theorem

The maximum power transfer theorem states that the maximum power is transferred to the load resistor  $R_L$  when the load resistance is equal to the Thevenin resistance  $R_{th}$  of the circuit.

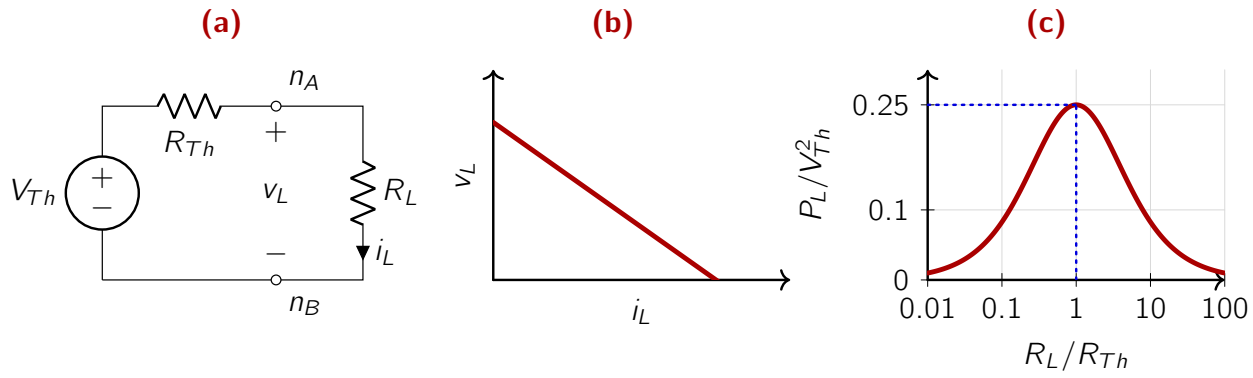

**Figure 2.6:** Maximum power transfer theorem.

Consider the following circuit (Figure 2.6). The power absorbed by the load resistor  $R_L$  is given by,

$$P_{R_L} = \frac{R_L}{(R_{th} + R_L)^2} V_{th}^2 \quad (2.24)$$

Its easy to check that the optimal value of  $R_L$  that maximizes the power absorbed by the load resistor is given by,

$$\begin{aligned} R_L^* &= \arg \max_{R_L} \frac{R_L}{(R_{th} + R_L)^2} V_{th}^2 = R_{Th} \\ P_L^* &= \max_{R_L} \frac{R_L}{(R_{th} + R_L)^2} V_{th}^2 = \frac{1}{4} \left( \frac{V_{Th}^2}{R_{Th}} \right) \end{aligned} \quad (2.25)$$