
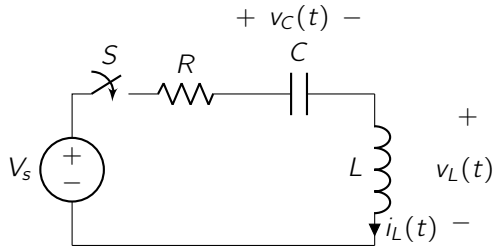


(a) A Simple RLC Circuit

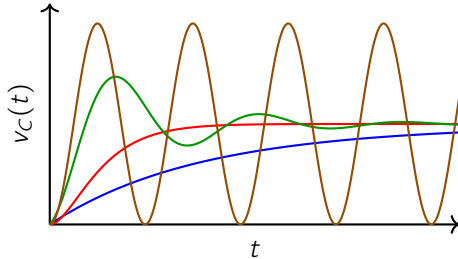

(b) Four different step responses



- Overdamped
- Critically damped
- Underdamped
- Undamped